

# B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

## December 2023 Supplementary Examinations

**Programme: B.E.**

**Branch: ECE/ML**

**Course Code: 22ES3PCNAL**

**Course: Network Analysis**

**Semester: III**

**Duration: 3 hrs.**

**Max Marks: 100**

**Instructions:** 1. Answer any FIVE full questions, choosing one full question from each unit.  
2. Missing data, if any, may be suitably assumed.

### UNIT - I

1 a) Apply mesh analysis and solve for voltage across  $3\text{k}\Omega$  for the circuit shown in **10**  
fig 1.1

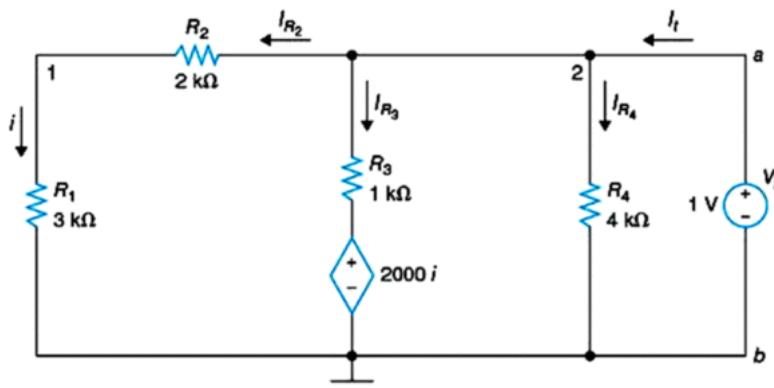


fig 1.1

b) For the network shown below, Use nodal analysis to find all node voltages **10**  
shown in fig 1.2

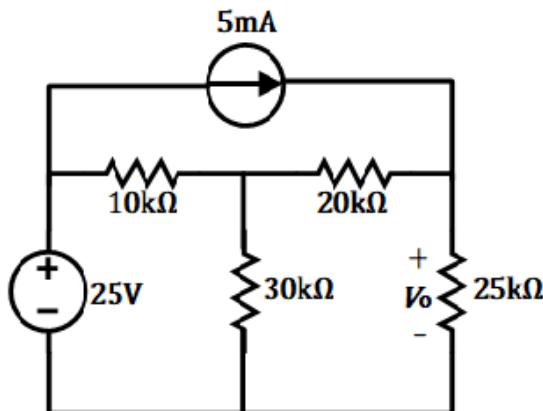


fig 1.2

**Important Note:** Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.

**OR**

2 a) Use mesh current method to find the power delivered by 10V source in the circuit shown in fig 2.1 10

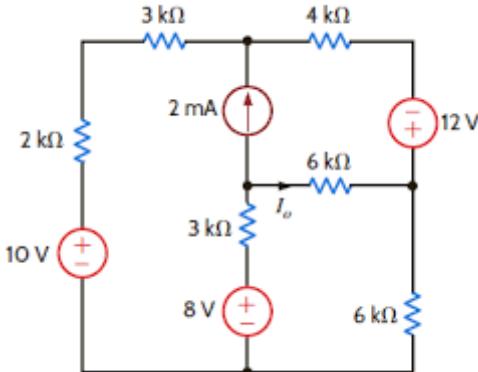


fig 2.1

b) Explain source transformation source shifting and Star Delta conversions with relevant examples 10

### UNIT - II

3 a) Derive the expression for the cutoff frequency, bandwidth and quality factor for a Series resonant circuit 10

b) A parallel resonance network has  $R=60\Omega$ ,  $C=120\mu F$  and  $L=200mH$  connected across voltage of 100v. Calculate  $f_0$ , B.W., Q factor and circuit current at resonance. 10

### UNIT - III

4 a) State and explain thevenin's theorem 05

b) Prove reciprocity theorem for the circuit shown in fig 4.1 08

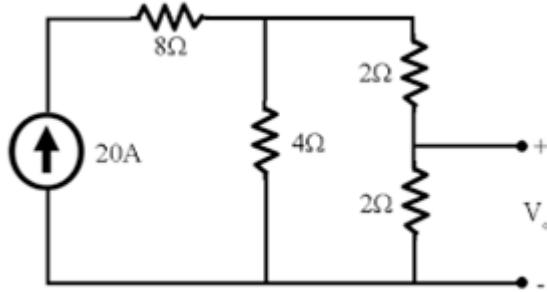


Fig 4.1

c) Find  $R_L$  for maximum power transfer for the circuit shown in fig 4.2 07


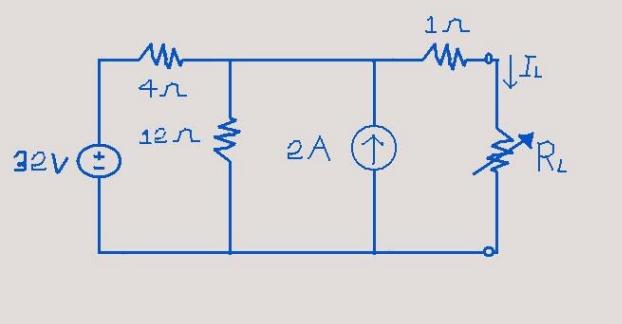


fig 4.2
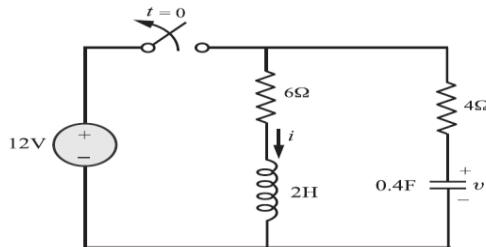
## UNIT - IV

5 a) A steady state is reached when switch k is closed. At  $t=0$  switch is opened. For the circuit shown in fig 5.1, find  $i(0+)$ ,  $V(0+)$  and  $di(0+)/dt$  10



b) Find the Laplace transform of the waveform shown in fig 5.2 10

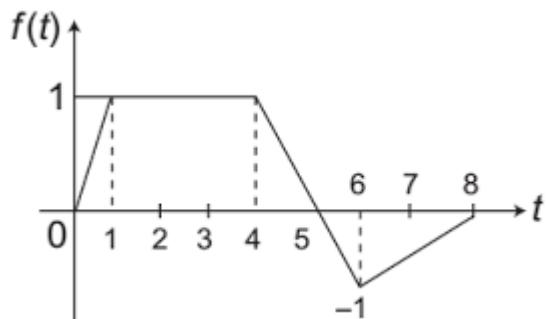


fig5.2

OR

6 a) Find the Laplace transform of the waveform given in fig 6.1 07

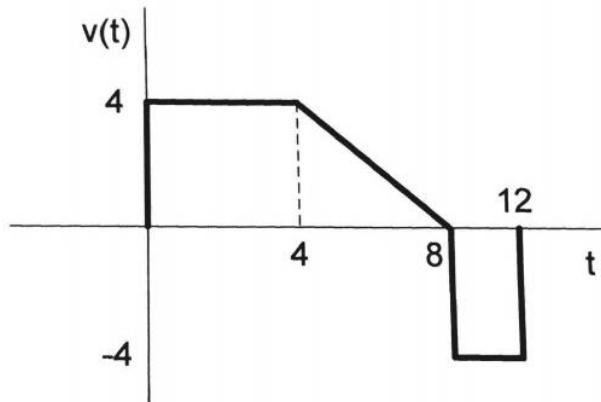


fig6.1

b) State and prove initial value theorem 05

c) For the network shown in fig 6.2 switch k is closed and steady state has been reached. At  $t=0$ , switch is opened. Find  $i(0+)$ ,  $di(0+)/dt$ ,  $d^2i(0+)/dt^2$  08

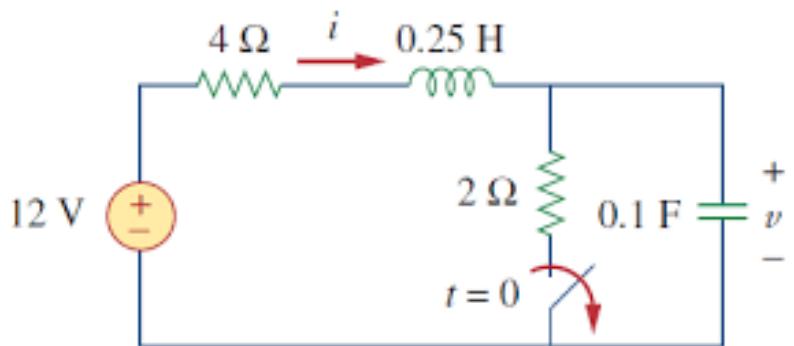


Fig 6.2

**UNIT - V**

7 a) Define T parameters. **04**  
 b) Obtain the relation between Z and h parameters **08**  
 c) For the circuit shown in fig 7.1 find T parameters. **08**

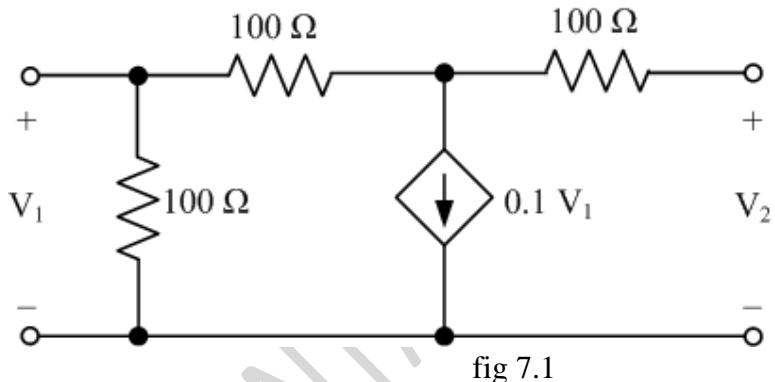


fig 7.1

\*\*\*\*\*