

# B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

## August 2023 Semester End Make-Up Examinations

Programme: B.E.

Branch: ECE/ML

Course Code: 22ES3PCNAL

Course: Network Analysis

Semester: III

Duration: 3 hrs.

Max Marks: 100


Date: 11.08.2023

**Instructions:** 1. Answer any FIVE full questions, choosing one full question from each unit.  
2. Missing data, if any, may be suitably assumed.

### UNIT - I


1 a) Apply mesh analysis and solve for  $V_0$  for the circuit shown in fig 1.1

10

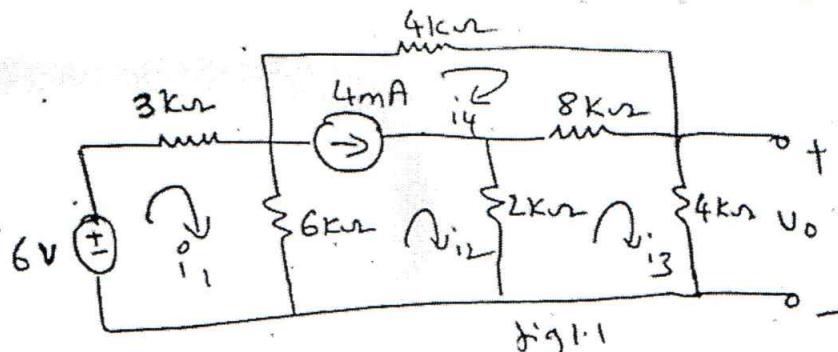

b) Use nodal analysis to find  $V_1$  and  $V_2$  for the circuit shown in fig 1.2


10

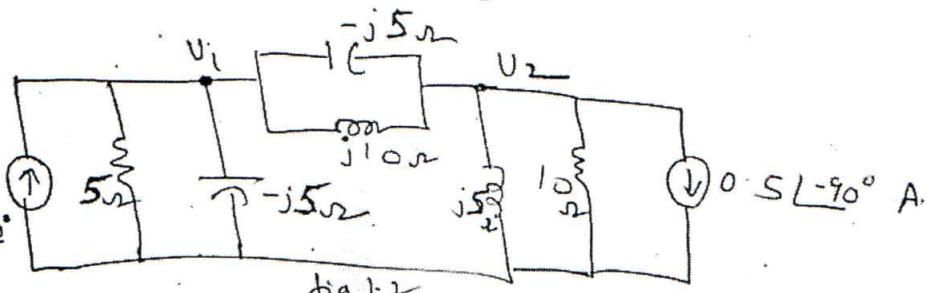


OR

2 a) Use mesh current method to find the power delivered by the dependent voltage source in the circuit shown in fig 2.1

10

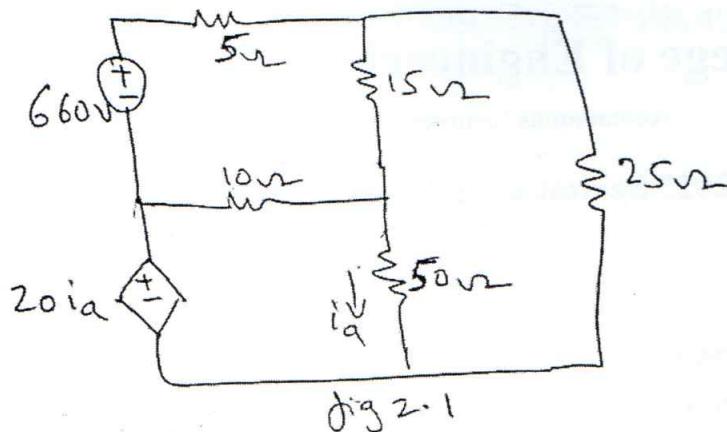

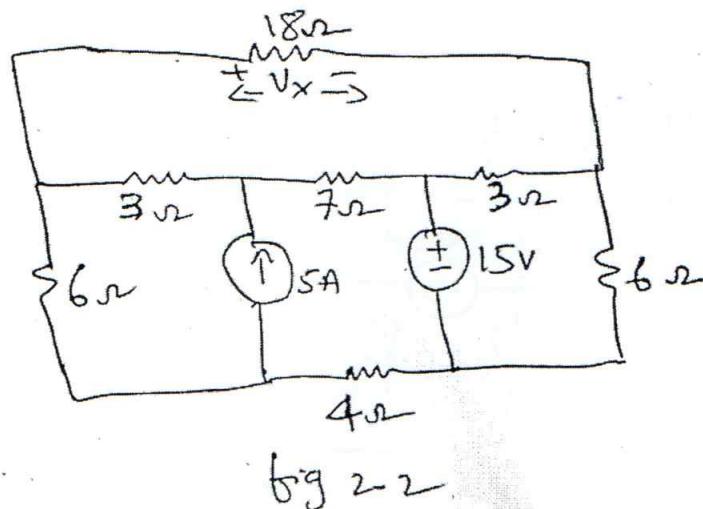b) Simplify the circuit shown in fig 2.2 using source transformation and source shifting and find the value of  $V_x$  10




## UNIT - II

3 a) Derive the expression for the cutoff frequency, bandwidth and quality factor for a series resonant circuit. 10


b) A parallel resonance network has  $R=60\Omega$ ,  $C=120\mu F$  and  $L=200mH$  connected across voltage of 100v. Calculate  $f_0$ , B.W., Q factor and circuit current at resonance. 10
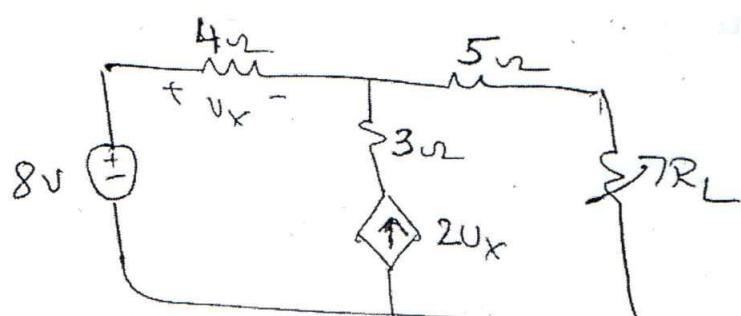
## UNIT - III

4 a) Determine the value of  $R_L$  for maximum power transfer and also calculate the value of maximum power. 07



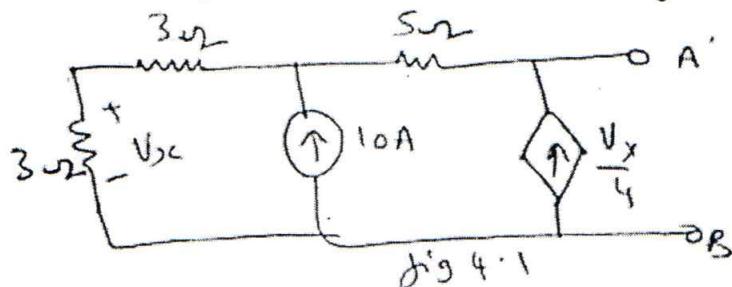b) State and prove reciprocity theorem. 07  
 c) Find the Norton equivalent of the network shown in fig 4.1 06



#### UNIT - IV

5 a) State and prove final value theorem. 05  
 b) A steady state is reached when switch K is at position 1. At  $t=0$  switch is moved from 1 to 2. Find  $i$ ,  $di/dt$  and  $d^2i/dt^2$  at  $t=0^+$  for the circuit shown in fig 5.1 10


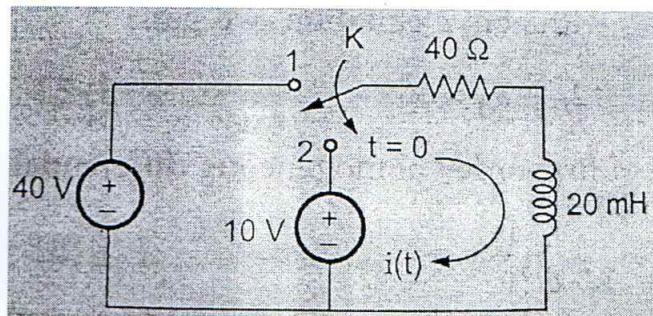



fig 5.1

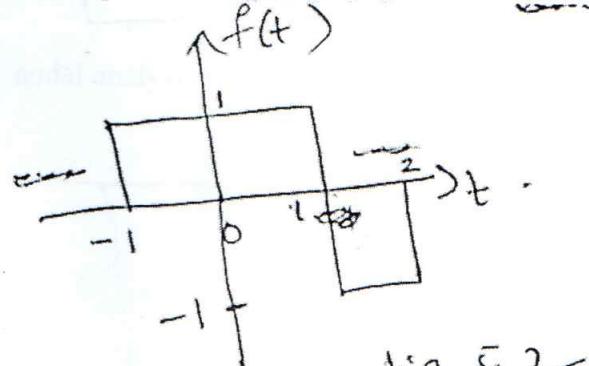c) Find the Laplace transform of the waveform shown in fig 5.2 05




OR

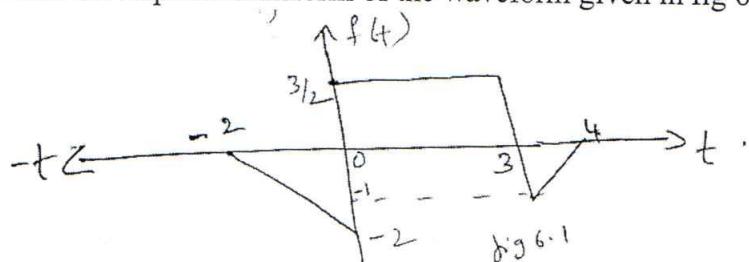6 a) Find the Laplace transform of the waveform given in fig 6.1 07




b) State and prove initial value theorem. 05

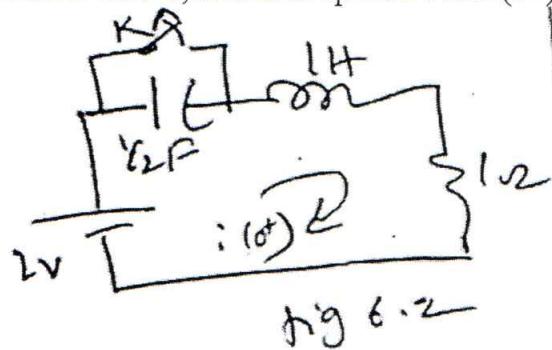c) For the network shown in fig 6.2 switch k is closed and steady state has been reached. At  $t=0$ , switch is opened. Find  $i(0+)$ ,  $di(0+)/dt$ ,  $d^2i(0+)/dt^2$  08



UNIT - V

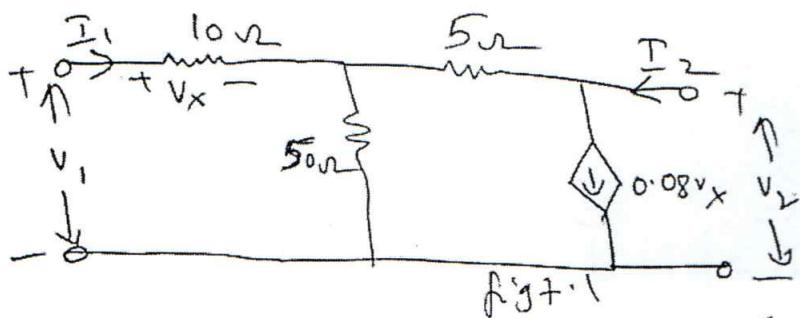7 a) Define h parameters. 04  
 b) Derive the relationship between Z and T parameter. 08  
 c) For the circuit shown in fig 7.1 find T parameters. 08



\*\*\*\*\*

B.M.Sc.E - 02