

# B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

## January / February 2025 Semester End Main Examinations

Programme: B.E.

Semester: III

Branch: EEE/ECE/MD/ETE/EIE



Duration: 3 hrs.

Course Code: 23ES3PCNAL

Max Marks: 100

Course: Network Analysis

- Instructions:** 1. Answer any FIVE full questions, choosing one full question from each unit.  
2. Missing data, if any, may be suitably assumed.

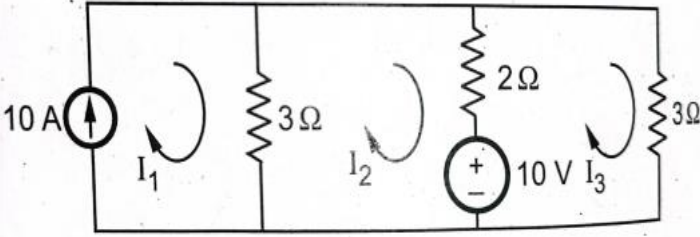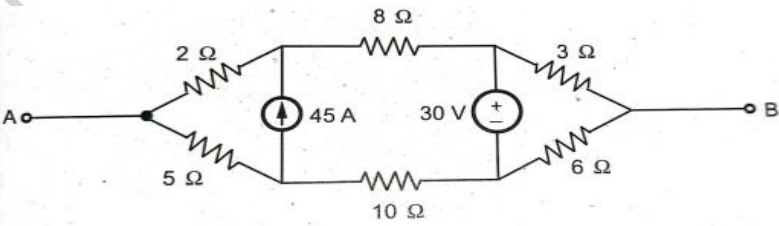		UNIT - I	CO	PO	Marks
<b>Important Note:</b> Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.	1	a) Define the following: (i) Active and passive elements, (ii) Independent and Dependent Sources, with Symbols.	CO1	PO1	5
		b) Write the mesh equation for the circuit shown in Fig 1.1 and determine mesh currents using mesh analysis.	CO1	PO1	8
		 <p style="text-align: center;">Fig 1.1</p>			
	c) Reduce the network shown in the Fig 1.2 to a single voltage source in series with a resistance using source shifting and source transformations.	CO1	PO1	7	
	 <p style="text-align: center;">Fig 1.2</p>				
		<b>OR</b>			
	2	a) Use the nodal analysis to calculate the value of $V_x$ in the circuit shown in the Fig 2.1 such that the current through $(2 + j3) \Omega$ impedance is zero.	CO1	PO1	10

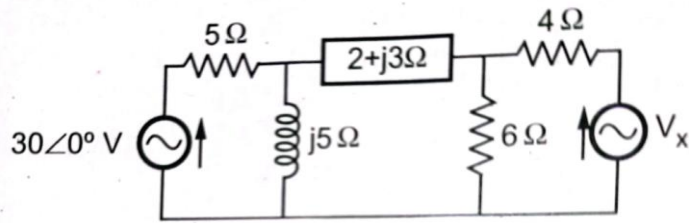


Fig 2.1

b) Explain the Concept of Super-mesh with an example.

C01

P01

5

c) Construct the dual of the network shown in Fig 2.2

C01

P01

5

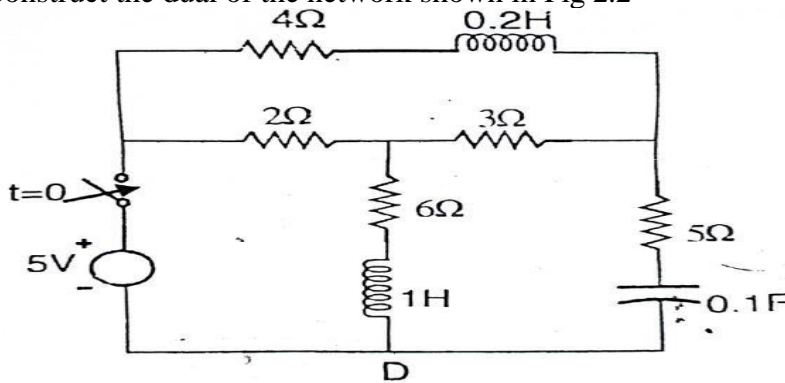


Fig 2.2

UNIT - II

3 a) Using Superposition Theorem, obtain the response 'I' for the network shown in Fig 3.1

C02

P02

10

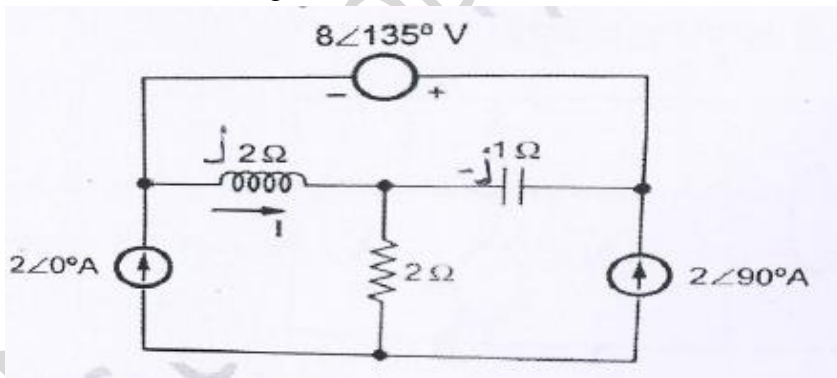


Fig 3.1

b) State and prove Thevenin's theorem.

C02

P02

10

OR

4 a) State and Prove Maximum Power transfer Theorem.

C02

P02

10

b) Calculate the current through the branch 'be' for the circuit given in Fig 4.1 using Norton's Theorem.

C02

P02

10

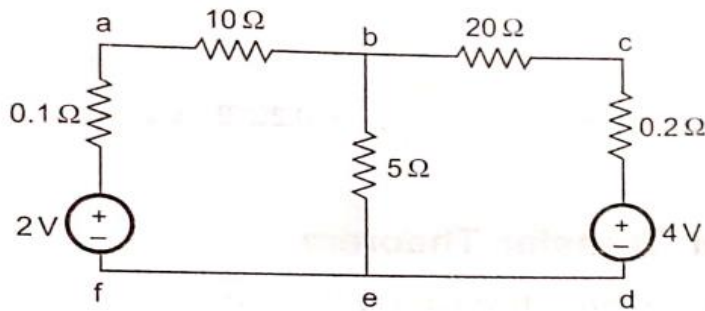


Fig 4.1

**UNIT - III**

- |   |    |   |     |     |    |
|---|----|---|-----|-----|----|
| 5 | a) | A series RLC circuit consists of $R=10\ \Omega$ , $L=0.01\ \text{H}$ , and $C=0.01\ \mu\text{F}$ is connected across a supply of $10\text{mV}$ . Determine, (i) $f_0$ ii) Q-factor iii) BW iv) $f_1$ and $f_2$ v) $I_0$ | CO2 | PO2 | 10 |
|   | b) | Explain parallel resonance. Derive the condition for parallel resonance when RL connected parallel to RC.   | CO2 | PO2 | 10 |

**OR**

- |   |    |  |     |     |    |
|---|----|--|-----|-----|----|
| 6 | a) | Define Q of a series resonant circuit. Obtain half power frequencies in terms of Q and show that the resonant frequency is the geometric mean of half power frequencies. | CO2 | PO2 | 10 |
|   | b) | For the parallel resonant circuit shown in Fig.6.1 Determine: $I_0$ , $I_L$ , $I_C$ , $f_0$ and dynamic resistance.  | CO2 | PO2 | 10 |

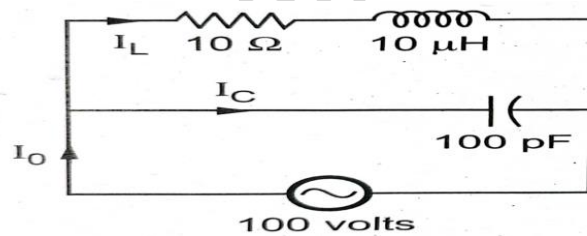


Fig.6.1

**UNIT - IV**

- |   |    |   |     |     |    |
|---|----|---|-----|-----|----|
| 7 | a) | State & prove Initial value theorem and Final value theorem.                  | CO2 | PO2 | 8  |
|   | b) | Determine the Laplace transform of the periodic waveform shown in the Fig 7.1 | CO2 | PO2 | 12 |

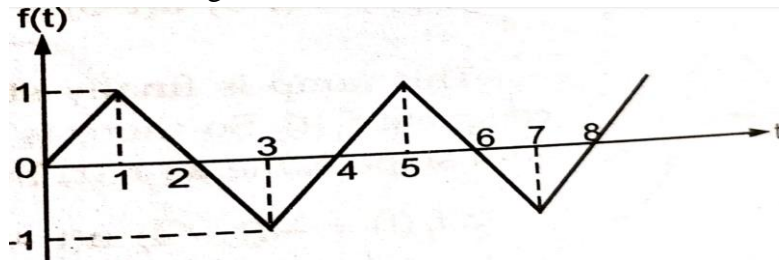


Fig 7.1

OR

8

a)

The network shown in the Fig.8.1 is under steady state condition with switch K is at position 1. Calculate expression for  $i(t)$  if switch K is moved to position 2. Draw variation of  $i(t)$ .

CO2

PO2

10

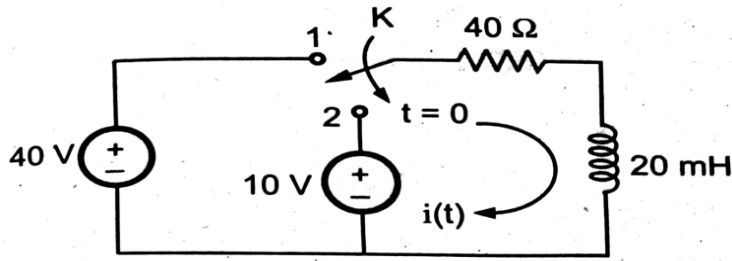


Fig.8.1

b)

Determine the Laplace transform of the periodic waveform shown in the Fig.8.2

CO2

PO2

10

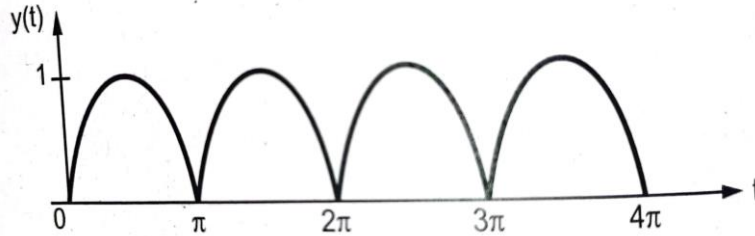


Fig.8.2

UNIT - V

9

a)

State and derive expressions for Z-Parameters or open circuit (O.C) Impedance Parameters.

CO2

PO2

10

b)

Define h-Parameter? and obtain the relationship between ABCD parameter in terms of Z-parameter.

CO2

PO2

10

OR

10

a)

Define Z and Y parameters. Obtain 'Z' Parameter in terms of 'Y' Parameters.

CO2

PO2

10

b)

Determine Y- parameters of the network shown in Fig.10.1

CO2

PO2

10

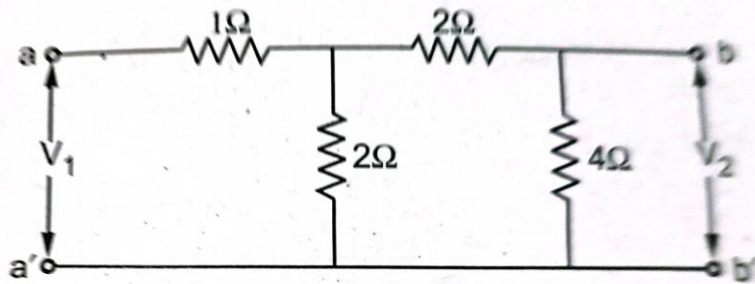


Fig 10.1

\*\*\*\*\*