

U.S.N.								
--------	--	--	--	--	--	--	--	--

B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

September / October 2024 Supplementary Examinations

Programme: B.E.

Branch: ES Cluster-EE, ECE

Course Code: 19ES4CCLIC

Course: Linear Integrated Circuits

Semester: IV

Duration: 3 hrs.

Max Marks: 100

Instructions: 1. Answer any FIVE full questions, choosing one full question from each unit.
2. Missing data, if any, may be suitably assumed.

UNIT - I			CO	PO	Marks
1	a)	Draw the equivalent circuit of op-amp. List ideal characteristics of op-amp.	CO1	PO1	04
	b)	Design a full wave precision rectifier circuit to get a positive pulsating DC output and explain its working. Draw the necessary waveforms.	CO1	PO2	08
	c)	For an inverting op-amp amplifier circuit $R_1 = 10 \text{ k}\Omega$, $R_2 = 100 \text{ k}\Omega$, $V_i = 1\text{V}$, $R_L = 25 \text{ k}\Omega$ Find (i) i_1 (ii) v_o (iii) i_L (iv) Total current I_o into the output pin.	CO1	PO1	08
OR					
2	a)	Explain working of instrumentation amplifier, obtain an expression for output voltage	CO1	PO1	08
	b)	Explain the working of 'voltage to current' converter with grounded load.	CO1	PO1	06
	c)	With a neat circuit diagram and waveforms, explain the working of peak detector circuit.	CO1	PO1	06
UNIT - II					
3	a)	With a neat circuit diagram, explain the working of Wein bridge oscillator.	CO2	PO1	06
	b)	Design an astable multivibrator using op-amp to generate a square wave of frequency 1 KHz and DC supply voltage of $\pm 12\text{V}$. Write the output waveforms.	CO2	PO2	08
	c)	Design a RC phase shift oscillator for a frequency of 1 KHz, assume $C = 0.01 \mu\text{F}$	CO2	PO2	06
UNIT - III					
4	a)	Explain the operation of a series voltage regulator, and any two of its Important performance parameters.	CO3	PO1	08
	b)	Design a II order Butterworth LPF for a cut-off frequency of 2KHz	CO3	PO2	06

Important Note: Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.

	c)	Discuss the technique of realizing higher order filters using lower-order filters.	CO3	PO1	06
		UNIT - IV			
5	a)	Define following specifications of D to A converter with suitable illustrations (i) Resolution (ii) Monotonicity (iii) Differential nonlinearity	CO4	PO1	06
	b)	A 8 bits D to A converter has a resolution of 10 mv/bit. Find the analog output voltage for inputs i) 10001010 ii) 01100011	CO4	PO2	04
	c)	Explain a 4 bits R-2R DAC, derive an expression for the output voltage in terms of binary inputs.	CO4	PO1	10
		OR			
6	a)	Implement a 2-bit flash type of A to D converter and explain its operation.	CO4	PO2	06
	b)	Differentiate between open-loop and closed-loop type ADCs with an example for each type.	CO4	PO1	04
	c)	Explain the operation of Successive approximation ADCs, with relevant illustrations.	CO4	PO1	10
		UNIT - V			
7	a)	With neat functional block diagram explain operation of 555 timer. Explain all the pin functions	CO5	PO1	08
	b)	Design a Monostable multivibrator using op-amp to obtain a pulse of width 10ms. Explain the operation	CO5	PO1	08
	c)	Briefly explain the application of PLL as a frequency multiplier.	CO5	PO1	04
