

U.S.N.								
--------	--	--	--	--	--	--	--	--

# B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

## August 2024 Semester End Main Examinations

**Programme: B.E.**

**Branch: Cluster (EIE/MD)**

**Course Code: 23ES4PCLIC**

**Course: Linear Integrated Circuits**


**Semester: IV**

**Duration: 3 hrs.**

**Max Marks: 100**

**Instructions:** 1. Answer any FIVE full questions, choosing one full question from each unit.  
2. Missing data, if any, may be suitably assumed.

<b>MODULE - I</b>			<b>CO</b>	<b>PO</b>	<b>Marks</b>	
<b>Important Note:</b> Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.	1	a)	With neat diagram, explain the blocks of an operational amplifier.	CO1	PO1	<b>05</b>
		b)	Discuss the DC Characteristic of an Op amp. List its typical values.	CO1	PO1	<b>08</b>
		c)	Suggest a three-op amp-based amplifier that can pick up the electric potential which is small in amplitude in presence of large noise from different sources. Also derive equation for gain of the amplifier.	CO1	PO1	<b>07</b>
<b>OR</b>						
	2	a)	Discuss the frequency response of an Op amp.	CO1	PO1	<b>07</b>
		b)	What is the highest frequency of a triangular wave of 20V peak to peak amplitude that can be reproduced by an Op amp whose slew rate is $10V/\mu s$ ? For a sine wave of same frequency, what is the maximum amplitude of output signal that remains undistorted?	CO2	PO2	<b>06</b>
		c)	Explain the working of series voltage regulator using Op amp with neat circuit diagram.	CO1	PO1	<b>07</b>
<b>MODULE - II</b>						
	3	a)	Derive an equations for amplitude and frequency of a triangular waveform for a triangular waveform generator.	CO2	PO2	<b>07</b>
		b)	Explain the working of 555 timer as a Monostable multivibrator with neat circuit diagram and waveforms.	CO1	PO1	<b>08</b>
		c)	Design and draw the circuit of a RC Phase shift oscillator for generating a frequency of 300Hz, assume $C = 0.1\mu F$ .	CO3	PO3	<b>05</b>
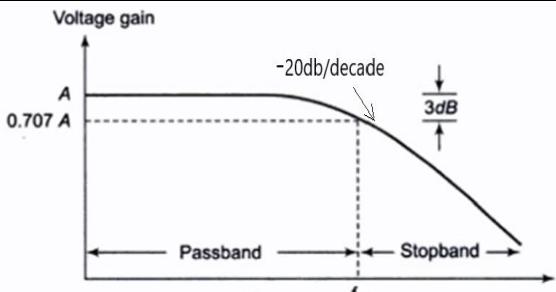
<b>MODULE - III</b>					
4	a)	 <p>Analyze the waveform shown, sketch a circuit using an op amp to obtain the output shown, also derive an equation for its transfer function.</p>	CO2	PO2	<b>10</b>
	b)	<p>Design a first order High pass filter having an upper cut off frequency of 2KHz with a pass band gain of 2. Also plot its frequency response.</p>	CO3	PO3	<b>10</b>
<b>MODULE - IV</b>					
5	a)	<p>Sketch the basic schematic of DAC. Also discuss the following specifications of DAC, (i) monotonicity and (ii) settling time.</p>	CO4	PO1	<b>07</b>
	b)	<p>Discuss the working of Successive approximation ADC with neat circuit diagram.</p>	CO4	PO1	<b>08</b>
	c)	<p>Find out the step size and analog output of a 4 bit R-2R ladder DAC when input is 1011 and 1001, assume V ref is 5V.</p>	CO4	PO2	<b>05</b>
<b>OR</b>					
6	a)	<p>Sketch the basic schematic of ADC. Also discuss the following specifications of ADC, (i) Resolution and (ii) conversion time</p>	CO4	PO1	<b>10</b>
	b)	<p>Discuss the working of a weighted resistor DAC with neat circuit diagram.</p>	CO4	PO1	<b>10</b>
<b>MODULE - V</b>					
7	a)	<p>Discuss the working of a phase locked loop with neat diagram. Also define (i)capture range (ii) Pull in time.</p>	CO1	PO1	<b>12</b>
	b)	<p>Suggest and explain circuit using PLL for the following            (i) Frequency translation            (ii) AM detector</p>	CO1	PO1	<b>08</b>

\*\*\*\*\*