

# B.M.S. College of Engineering, Bengaluru-560019

Autonomous Institute Affiliated to VTU

## February 2025 Semester End Main Examinations

**Programme: B.E.**

**Branch: ES Cluster (EIE/MD)**

**Course Code: 23ES4PCLIC / 22ES4PCLIC**

**Course: Linear Integrated Circuits**

**Semester: IV**

**Duration: 3 hrs.**

**Max Marks: 100**

**Instructions:** 1. Answer any FIVE full questions, choosing one full question from each unit.  
2. Missing data, if any, may be suitably assumed.


<b>MODULE - I</b>			<b>CO</b>	<b>PO</b>	<b>Marks</b>
1	a)	Discuss the DC characteristics of op amp with typical values	<i>CO1</i>	<i>PO1</i>	<b>08</b>
	b)	Discuss the working of a circuit using op amp to obtain the positive pulsating DC output.	<i>CO1</i>	<i>PO1</i>	<b>06</b>
	c)	A square wave of peak to peak amplitude of 500mv has to be amplified to peak to peak amplitude of 3volts with rise time of 5 $\mu$ s or less. Can a 741 be used?	<i>CO2</i>	<i>PO2</i>	<b>06</b>
<b>OR</b>					
2	a)	Discuss Frequency response of an Op amp	<i>CO2</i>	<i>PO2</i>	<b>07</b>
	b)	Explain the working of an I-V converter with a neat circuit diagram.	<i>CO1</i>	<i>PO1</i>	<b>06</b>
	c)	Analyze the waveforms and suggest a circuit to obtain the output shown	<i>CO2</i>	<i>PO2</i>	<b>07</b>
<b>MODULE - II</b>					
3	a)	Derive an equation for obtaining amplitude and frequency of the Astable multivibrator using analog integrated device.	<i>CO2</i>	<i>PO2</i>	<b>10</b>
	b)	Obtain an equation for frequency of oscillation and gain for sustained oscillations for RC phase shift oscillator	<i>CO2</i>	<i>PO2</i>	<b>10</b>
<b>OR</b>					



**Important Note:** Completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages. Revealing of identification, appeal to evaluator will be treated as malpractice.

Output

**MODULE - II**

**OR**

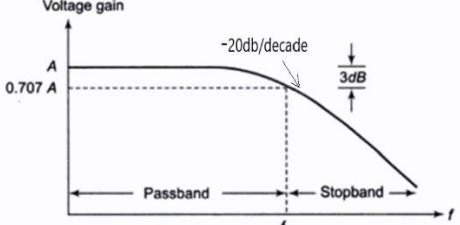4	a)	Discuss with neat circuit, Equations and waveforms the working of Schmitt trigger	CO2	PO1	<b>09</b>
	b)	Design and draw the circuit of a Wein bridge oscillator for generating a frequency of 2KHz, assume $C = 0.05\mu F$ .	CO3	PO2	<b>06</b>
	c)	With a neat circuit diagram, explain the working of a zero-crossing detector	CO1		<b>05</b>
	<b>MODULE - III</b>				
5	a)	Derive the transfer function of a variable gain High pass filter with relevant circuit and equation.	CO3	PO3	<b>10</b>
	b)	Design a fourth order Butterworth low pass filter having upper cut off frequency of 1KHz, $\alpha_1 = 0.765$ and $\alpha_2 = 1.848$ .	CO3	PO3	<b>10</b>
	<b>OR</b>				
6	a)	 <p>Analyze the waveform shown, sketch a circuit using an op amp to obtain the output shown, also derive an equation for its transfer function.</p>	CO2	PO1	<b>10</b>
	b)	Design a first order High pass filter having an upper cut off frequency of 2KHz with a pass band gain of 2. Also plot its frequency response.	CO3	PO2	<b>10</b>
	<b>MODULE - IV</b>				
7	a)	Sketch the basic schematic of DAC. Also discuss the following specifications of DAC, (i) monotonicity and (ii) settling time	CO4	PO1	<b>07</b>
	b)	Explain the working of a Counter type ADC	CO4	PO1	<b>08</b>
	c)	A 12-bit DAC has a step size of 8mV. Determine the full-scale output voltage and percentage resolution. Also find the output voltage for an input voltage of 100110011101.	CO4	PO2	<b>05</b>
	<b>OR</b>				
8	a)	Sketch the basic schematic of ADC. Also discuss the following specifications of ADC, (i) Resolution and (ii) conversion time	CO4	PO1	<b>07</b>
	b)	Sketch the circuit and discuss the working principle for the weighted resistor DAC	CO4	PO1	<b>08</b>
	c)	The resolution of a 4-bit counting ADC is 0.6 volts. For an analog input of 5.5volts, what will be the output of the ADC?	CO4	PO2	<b>05</b>
	<b>MODULE - V</b>				
9	a)	Sketch the basic block of PLL. Also discuss the following specifications of PLL, (i) Lock in range and (ii) pull in time.	CO1	PO1	<b>10</b>

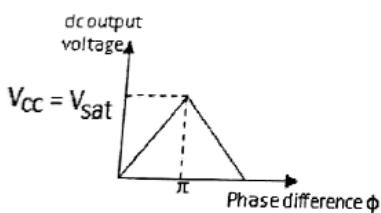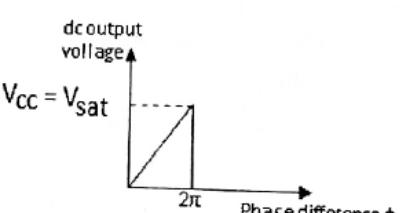	b)	Suggest circuit using PLL for (i) Frequency translation (ii) Frequency division	CO1	PO1	<b>10</b>
		<b>OR</b>			
10	a)	Identify and explain the suitable blocks of PLL which has following transfer characteristics as shown below.	CO2	PO1	<b>10</b>
	b)	  <p>Describe the working principle of Voltage Controlled Oscillator with neat block diagram</p>	CO1		<b>10</b>

\*\*\*\*\*